

CONTENTS - Valves for Audio Frequency Amplifiers by E. Rodenhuis - code 2002

title	page No.
THE DESIGN OF AN AUDIO FREQUENCY AMPLIFIER	1
Preface	1
Chapter I. GENERAL HINTS ON AMPLIFIER CONSTRUCTION	3
1. Mounting the components	8
2. Assembly and wiring	8
3. Summary of general hints	9
Chapter II. THE VALVES FOR THE VARIOUS STAGES	11
1. Pre-amplifier valves	12
2. Phase inverters	12
3. Output valves	14
4. Rectifier valves	14
Chapter III. DESCRIPTION OF THE VALVES EF40, EF86, ECC40, ECC83, EL34, EL84 and GZ34	16
EF 40, A.F. pentode with low noise level	20
Valve data of the A.F. pentode EF 40	20
EF 86, A.F. pentode with low noise level	22
Technical data of the A.F. pentode EF 86	23
Double triode ECC 40	26
Valve data of the double triode ECC 40	27
The ECC 40 operated as power valve	32
The ECC 40 a8 amplifier and phase inverter	32
ECC 83, high-mu double triode	37
Valve data of the high mu double triode ECC 83	38
EL 34, power pentode	49
Valve data of the power pentode EL 34	49
EL 84, output pentode	59
Valve data of the output pentode EL 84	60
GZ 34 high-vacuum full-wave rectifier	61
Valve data of the high-vacuum full-wave rectifier GZ 34	63
Chapter IV. HINTS ON PRACTICAL USES OF THE VALVE DATA	66
	66
Chapter V. COMPONENTS AND CIRCUITS	67
1. Negative feedback	67
2. Negative feedback dependent on frequency	68
3. Tone control	70
4. The output transformer	72
5 The input of the amplifier and the volume control	79
tf. Microphones, pick-ups and loudspeakers	79
Chapter VI. DETAILS OF SOME AMPLIFIER CIRCUITS	79

1. A 3 W GRAMOPHONE AMPLIFIER	83
Circuit description	83
2. A HIGH-FIDELITY AMPLIFIER WITH TWO TUBES EL 84 IN PUSH-PULL	85
Circuit description	93
Measured results	93
3. A 10 W CLASS A AMPLIFIER WITH THE EL 34 AS OUTPUT VALVE	95
Circuit description	99
Measured results	100
4. A 15 W A.C./D.C. AMPLIFIER WITH TWO VALVES TYPE PL 81 IN CLASS B PUSH-PULL CIRCUIT	102
Circuit description	107
Measured results	107
5. A 35 W AMPLIFIER WITH TWO EL 34 VALVES IN CLASS AB PUSH-PULL	110
Circuit description	115
Measured results	115
6. A 35 W QUALITY AMPLIFIER WITH TWO EL 34 VALVES IN CLASS AB	117
Circuit description	121
Measured results	121
7. A 70 W QUALITY AMPLIFIER WITH FOUR EL 34 VALVES IN CLASS AB PUSH-PULL	122
Circuit description	127
Measured results	127
8. A 100 W AMPLIFIER WITH TWO EL 34 OUTPUT VALVES IN CLASS B	130
Circuit description	
Measured results	